 


Digital systems

- Digital systems is one where both the input and the output are digital signals.
- It is widely used in.
 - Operate in one of the 2 states ON/OFF, resulting in simple circuit operation.
 - Can be realized as integrated circuits which are highly reliable, extremely small in size and cost very less.

Digital circuits


- Involves circuit that has 2 possible states i.e., Binary system.
- The operation of the circuit can be described in terms of its voltage level.
 - two voltage levels High or low.



- Digital circuits can be of two types.


- Positive logic

 - Choose the high-level H as logic 1
- Choose the low-level L as logic 0



- Negative logic

 - Choose the high-level H as logic 0
- Choose the low-level L as logic 1



Logic gates:


Logic gates are electronic circuit's elements that perform the corresponding logical operations.

Properties of logic gates:

- logic gates handle binary signals and also generate binary signals.
- logic gates can have more than 2 inputs.


Basic gates

 AND Gate: Produces 1 at the o/p if both the inputs X and Y change to 1




A	B	O/P(Y)
0	0	0
0	1	0
1	0	0
1	1	1

 OR gate: Produces the o/p 1 if either of the logic states of inputs A and B change of 1.



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 NOT gate: Reverses the input and also known as inverter.




A	$\bar{A}$
0	1
1	0

EX-OR gate: The o/p of an EX-OR gate gives "HIGH" only when both of its input terminals are at "DIFFERENT" logic levels with respect to each other. It implements the function "A OR B but NOT both".




A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 EX-NOR gate: The output of an EX-NOR gate gives "HIGH" when both of its input terminals are at "SAME" logic levels with respect to each other and is also known as equivalence gate.




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

 NAND gate: It has the opposite o/p to the AND gate. It is NOT-AND.




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 NOR gate: It has the opposite of the OR gate.
It is NOT-OR.




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

De Morgan's Theorem

 

 A NAND gate is equivalent to an inversion followed by an OR.



A NOR gate is equivalent to an inversion followed by an AND.

Boolean Laws

Law / Theorem	Law of Addition	Law of Multiplication
Identity law	$x + 0 = x$	$x \cdot 1 = x$
Complement law	$x + x' = 1$	$x \cdot x' = 0$
Idempotent law	$x + x = x$	$x \cdot x = x$
Dominant law	$x + 1 = 1$	$x \cdot 0 = 0$
Involution law	$(x')' = x$	
Commutative law	$x + y = y + x$	$x \cdot y = y \cdot x$
Associative law	$x + (y + z) = (x + y) + z$	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$
Distributive law	$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + y \cdot z = (x + y) \cdot (x + z)$
Demorgan's law	$(x + y)' = x' \cdot y'$	$(x \cdot y)' = x' + y'$
Absorption law	$x + (x \cdot y) = x$	$x \cdot (x + y) = x$


Definition of Combinational logic

• combinational logic deals with the techniques of "combining" the basic gates into circuits that perform some desired function.


eg: Adders, Subtractors, Decoders, Encoders, Multiplexers

• logic circuits without feedback from output to input.

• logic circuits that contain no memory.

 

General logic Design sequence:

 


Combinational logic Specification

1] Logic Diagram: Graphical representation.

2] Truth table: A list that shows all the o/p states in tabular form for each possible combination of input variable.

3] Boolean Equations: Algebraic expressions showing the operation of the logic circuit for each input variable.

Logic Gates & Logic Diagram

 

Boolean Expression:

$$Q = (A \cdot B) \cdot (A + B) \cdot C$$

Typical Truth table:

C	B	A	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Boolean Equations or Switching equations:

- A literal is a Boolean variable or its complement (a, x', z')
- A product term is a literal or the logical product (AND) of multiple literals ($ab, x'y, z'y'$)
- A sum term is a literal or the logical sum (OR) of multiple literals ($a+b, a'+b, x'+y'$)
- A sum of product (SOP) is the logic OR of multiple product terms ($ab+bc'+d'b'$)

- A product of sum (Pos) is the logical AND of multiple sum terms $[(a+b')(a'+b')(a+b)]$

Minterms

- A minterm is a special product of literals, in which each input variable appears exactly once.
- A function with n variables has 2^n minterms.
- Each minterm is true for exactly one combination of i/p's

Minterm	Is true when ...	Shorthand
$x'y'z'$	$x=0; y=0; z=0$	m_0
$x'y'z$	$x=0; y=0; z=1$	m_1
$x'yz'$	$x=0; y=1; z=0$	m_2
$x'yz$	$x=0; y=1; z=1$	m_3
$xy'z'$	$x=1; y=0; z=0$	m_4
$xy'z$	$x=1; y=0; z=1$	m_5
xyz'	$x=1; y=1; z=0$	m_6
xyz	$x=1; y=1; z=1$	m_7

Sum of Minterms

X	Y	Z	$f(x,y,z)$	$f'(x,y,z)$
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

$$\begin{aligned}
 f &= x'y'z' + x'y'z + x'yz' + x'yz + xy'z' \\
 &= m_0 + m_1 + m_2 + m_3 + m_4 \\
 &= \sum m(0, 1, 2, 3, 4)
 \end{aligned}$$

$$\begin{aligned}
 f' &= x y z' + x y' z + x y z \\
 &= m_4 + m_5 + m_7 \\
 &= \sum m (4, 5, 7)
 \end{aligned}$$

f' contains all the minterms not in f .

Maxterms

- A maxterm is a special sum of literals, in which each input variable appears exactly once.
- A function with n variables has 2^n maxterms.
- Each maxterm is false for exactly one combination of inputs.

Maxterm	Is false when...	Shorthand
$x + y + z$	$x=0; y=0; z=0$	M_0
$x + y + z'$	$x=0; y=0; z=1$	M_1
$x + y' + z$	$x=0; y=1; z=0$	M_2
$x + y' + z'$	$x=0; y=1; z=1$	M_3
$x' + y + z$	$x=1; y=0; z=0$	M_4
$x' + y + z'$	$x=1; y=0; z=1$	M_5
$x' + y' + z$	$x=1; y=1; z=0$	M_6
$x' + y' + z'$	$x=1; y=1; z=1$	M_7

Product of Maxterms.

x	y	z	$f(x, y, z)$	$f'(x, y, z)$
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

$$\begin{aligned}
 f &= (x' + y + z)(x' + y + z')(x' + y' + z') \\
 &= M_4 M_5 M_7 \\
 &= \Pi M(4, 5, 7)
 \end{aligned}$$

$$\begin{aligned}
 f' &= (x + y + z)(x + y + z')(x + y' + z)(x + y' + z') \\
 &\quad (x' + y' + z)
 \end{aligned}$$

$$= M_0 M_1 M_2 M_3 M_6$$

$$= \Pi M(0, 1, 2, 3, 6)$$

f' contains all the maxterms not in f .

Relation of Minterm to Maxterm.

- Any minterm m_i is the complement of the corresponding maxterm M_i

Minterm	Shorthand	Maxterm	Shorthand
$x'y'z'$	m_0	$x+y+z$	M_0
$x'y'z$	m_1	$x+y+z'$	M_1
$x'y z'$	m_2	$x+y'z$	M_2
$x'y z$	m_3	$x+y'+z'$	M_3
$x y'z'$	m_4	$x'+y+z$	M_4
$x y'z$	m_5	$x'+y+z'$	M_5
$x y z'$	m_6	$x'+y'+z'$	M_6
$x y z$	m_7	$x'+y'+z$	M_7

Canonical Forms.

- A canonical form of a switching equation is one that contains all of the available input variables.
- > Canonical Sum of Products: It is a complete set of minterms that defines when an output is a logical 1.
- > Canonical Product of sums: It is a complete set of maxterms that defines when an output is a logical 0.

- Canonical expressions are not simplified and contains redundancies.

$f = x'y' + x'y + xyz'$ is a normal expression.
 $x'y'z' + x'y'z + x'yz' + x'yz + xyz'$ is the canonical form.

Conversion to Canonical form:

- SOP to canonical:
 - > Identify the missing variable in each AND term.
 - > AND the missing term and its complement with the original AND term.
 - > Expand the term by distribution property.
- POS to canonical:
 - > Identify the missing variable in each OR term.
 - > OR the missing term and its complement with the original OR term.
 - > Expand the term by distribution property.

Grouping in KMap:

Rules of grouping:

- 1's & 0's can not be grouped
- diagonal 1's can not be grouped.
- Elements in a grp should be 2^n .
- Minimum grp should be formed.
- Overlapping is applicable.

The three variable KMap.

	ab	a'b'	a'b	ab'
c	00	01	11	10
c'0	000 0	010 2	110 6	100 4
c'1	001 1	011 3	111 7	101 5

Don't care Conditions.

- In some cases, the function is not specified for certain combinatⁿ of input variables as 1 or 0.
- There are 2 cases in which it occurs.
 - The input combination never comes.
 - The input combination occurs but we do not care what the outputs are in response to these inputs because the output will not be observed.
- In both cases, the outputs are called as unspecified and the functions having them are called as incompletely specified functions.
- In most applicatⁿs, we simply do not care what value is assumed by the functions for unspecified minterms.
- A don't care condition, marked by (x) in the truth table or excess 3 code converter ($\frac{1}{2}$) table, indicates a condition where the design doesn't care if the output is a (0) or (1).
- A don't care condition can be treated as a (0) or a (1) in a k-map.
- Treating a don't care as a (0) means that you do not need to group it.
- Treating a don't care as a (1) allows you to make a grouping larger, resulting in a simplified term in the SOP equation.

BCD to Excess 3 code Converter ($\frac{1}{2}$)

Truth table:

	BCD				Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	0	0	0
2	0	0	1	0	0	0	0	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	0	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

K Map:

W

AB	C			
	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

X

AB	C			
	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X

Y

AB	C			
	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	X	X	X	X
10	1	0	X	X

Z

AB	C			
	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X

$$W = A + BC + BD = A + B(C + D)$$

$$X = B'C + B'D + BC'D$$

$$= B'(C + D) + BC'D$$

$$Y = CD + C'D$$

$$Z = D'$$

Logic Diagram

